

## Stacked amplifiers lower noise

Scott Wurcer and Charles Kitchin  
Analog Devices Inc, Wilmington, MA


You can realize an improvement in the signal-to-noise ratio of an amplification system by stacking the system's amplifiers—connecting their inputs in parallel and their outputs in series. In this configuration, the combined S/N ratio improves in direct proportion to the square root of the number of amplifiers stacked. This improvement arises because the signals add arithmetically while the combined noise only increases as the square root of the number of amplifiers. However, it occurs only if the source voltage is not decreased by loading.

Stacked amplifiers have not been extensively used because of hardware considerations: You need transformers to add the outputs. However, if you use instrumentation amplifiers, you can add the outputs by feeding one amplifier's output into the reference input of the next.


The AD524 instrumentation amplifier is particularly well suited for this purpose. It features programmable gain, low noise, high input impedance and wide-band response. **Fig 1** shows two AD524s configured in the stacked configuration, providing a 3-dB increase in S/N ratio compared with one amplifier. You can achieve a final improvement in the S/N ratio by using the 524's ultralow-noise version, the AD624, which features a 4-nV/ $\sqrt{\text{Hz}}$  front end.

You can also modify **Fig 1**'s circuit to produce an active balanced transformer (**Fig 2**). This circuit provides the same 3-dB noise improvement because,

*Continued on pg 185*

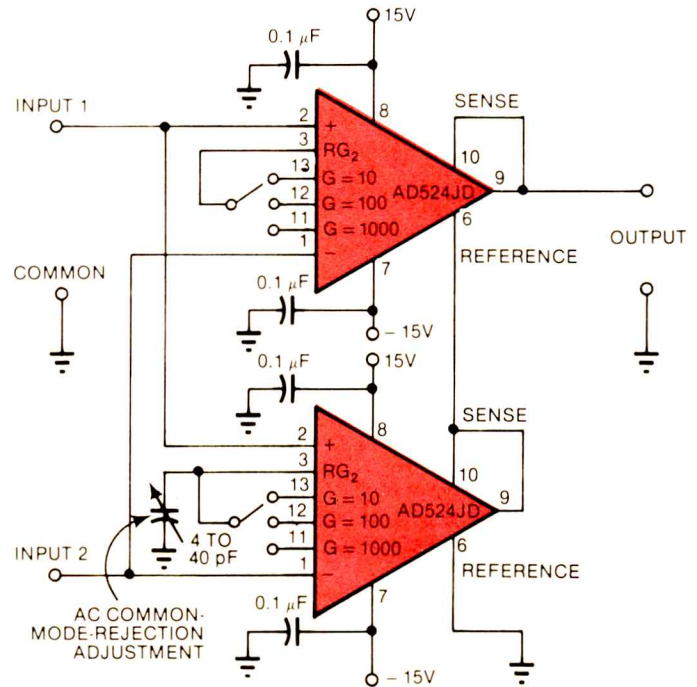

**Fig 1**—Stack two instrumentation amplifiers to obtain a 3-dB improvement in S/N ratio. The output of one feeds into the reference input of the next, so the output levels add.

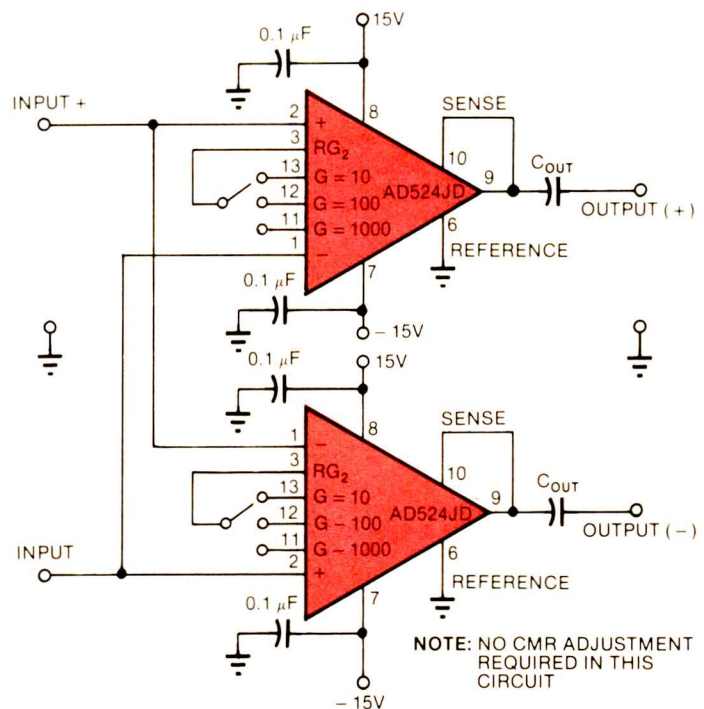

**Fig 2**—Modify **Fig 1**'s circuit to form an active balanced transformer. This arrangement still realizes the improvement in S/N ratio that's characteristic of stacked amplifiers.

### COMPARATIVE PERFORMANCE OF FIG 1 AND FIG 2 CIRCUITS

PARAMETER	FIG 1	FIG 2
SLEW RATE	5V/ $\mu\text{SEC}$	10V/ $\mu\text{SEC}$
MAX OUTPUT LEVEL	20V P-P (7.1V RMS)	40V P-P (14.2V RMS)
- 3-dB BANDWIDTH AT 1V P-P OUTPUT FOR GAIN = 2 (6 dB) FOR GAIN = 20 (26 dB) FOR GAIN = 200 (46 dB) FOR GAIN = 2000 (66 dB)	DC-850 kHz DC-380 kHz DC-200 kHz DC-30 kHz	DC-1 MHz DC-500 kHz DC-200 kHz DC-30 kHz
COMMON-MODE REJECTION RATIO (GAIN = 2, 20V P-P SINE WAVE COMMON-MODE INPUT LEVEL)	-80 dB AT 60 Hz -80 dB AT 10 kHz (WITH CMR TRIM)	-93 dB AT 60 Hz -83 dB AT 10 kHz
NOISE IN 20-kHz BANDWIDTH	0.6 $\mu\text{V}$ RETURNED TO INPUT	0.6 $\mu\text{V}$ RETURNED TO INPUT
TOTAL HARMONIC DISTORTION	< 0.01%	< 0.01%

## Design Entry Blank

**\$40 Cash Award for all entries selected by editors. An additional \$75 Cash Award for winning design each issue, determined by vote of readers. Additional \$1000 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.**

To: Design Ideas Editor  
EDN  
Cahners Publishing Co  
221 Columbus Ave, Boston, MA 02116

I hereby submit my entry for  
EDN's Design Ideas program.

Name \_\_\_\_\_

Title \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Division (if any) \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Design Title \_\_\_\_\_

Home Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Social Security No \_\_\_\_\_

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_

Date \_\_\_\_\_

**Your vote determines this issue's winner.** All designs published win \$40 cash. All issue winners receive an additional \$75 and become eligible for the annual \$1000 Grand Prize.

**Vote now**, by circling the appropriate number on the reader inquiry card.

**Submit your own design**, too. Mail entries to Design Ideas Editor, EDN, 221 Columbus Ave, Boston, MA 02116.

as in Fig 1, the signals add but the noise outputs don't correlate.

Note that Fig 2's circuit, unlike a conventional transformer, does not provide galvanic isolation between its input and output unless both are ac coupled. In addition, if the inputs are ac coupled, you must provide a return path to ground via two large-value input resistors connected between each input and ground. The value of these resistors should be several times the source impedance. **EDN**


### To Vote For This Design, Circle No 452
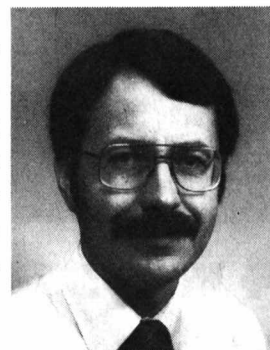
#### Readers have voted:

**Ron Burski** winner of the January 20, 1982 issue's \$75 award for best design. His design is "Optical sensor ignores ambient light." Mr Burski is with Dataproducts, Woodland Hills, CA.



**Paul E Schulze** winner of the February 3, 1982 issue's \$75 award for best design. His design is "Timer protects CRT phosphors." Mr Schulze is with Xerox Electro-Optical Systems, Pasadena, CA.



**Peter Winship** winner of the February 17, 1982 issue's \$75 award for best design. His design is "Two diodes provide a 99:1 cycle." Mr Winship resides in Berkeley, CA.

**Stephen Cannon** winner of the March 17, 1982 issue's \$75 award for best design. His design is "Decoder forms mutually exclusive latch." Mr Cannon is with Corometrics Medical Systems, Wallingford, CT.

