

APPLICATION NOTE 4708

LED driver solution for MR16 and similar retrofit lamps

By: Piero Bianco

Abstract: This application note presents an LED driver solution for MR16 and similar retrofit lamps. The circuit drives LEDs from a 12VAC input. The solution works with both magnetic and electronic transformers and is dimmable. It requires no electrolytic capacitors, which extends LED lamp life. Test setup and results are shown.

Introduction

This application note describes a proprietary solution that will drive LEDs off a 12VAC input for MR16 and similar retrofit lamps. This design can be used with both magnetic and electronic transformers. It is dimmable with leading-edge dimmers for magnetic transformers and with trailing-edge dimmers for electronic transformers. No electrolytic capacitors are required. This greatly extends the lifetime of an LED lamp, because electrolytic capacitors are typically the element of the system with the shortest lifetime.

Solution specifications

- Input voltage: 12VAC
- Output LED power: 5W
- Number of output series LEDs: 3 to 4

Board terminals (Figure 1)

- Inputs: V_{IN1} , V_{IN2} , input AC supply
- Outputs: LED+, LED-, output LED anode and cathode connections

dimmers are typically used, because leading-edge (i.e., triac) dimmers do not work correctly with electronic transformers.

Trailing-edge dimmers reduce the amount of lamp light by cutting the final part of the line voltage at each half cycle.

Sometimes the infrastructure still includes a magnetic transformer instead of an electronic one. A magnetic transformer has the same requirements for resistive behavior of the load and minimum load current as does an electronic transformer. However, if a dimmer is present (leading-edge dimmers are typically used with magnetic transformers), the dimmer requires a resistive load and a minimum load current. In short, the LED driver has similar constraints to those mentioned above for electronic transformers.

Description of the circuit

This circuit is a buck-boost converter, composed of inductor L1, switching MOSFET Q1, and power diode D6. It works in fixed-frequency, continuous-conduction mode.

The solution presented here uses an active, power factor correction (PFC) approach to control and shape the input current so it is compatible with electronic transformers and dimmers. Active PFC provides the best control of the input current; it keeps the current above the minimum required by the dimmer and transformer for the largest part of the input voltage cycle and, thus, avoids transient spikes of that current. Active PFC is, therefore, the best approach to design a dimmable lamp with no flicker.

Active PFC does not require large value (i.e., electrolytic) input capacitors. This is an advantage of the design. In this solution the input capacitor (C2) is a small value and ceramic. This solution works without electrolytic capacitors, which considerably extends the lamp lifetime.

LEDs dissipate most of the power provided to them by conduction. Meanwhile, MR16 LED lamps have little space for heatsinks because of their small size. Consequently, they often run at high temperatures in the +80°C to +100°C range. At those temperatures, even the lifetime of high-grade electrolytic capacitors is limited to little more than 10,000 hours, which is too few hours for an LED lamp.

Active PFC in this solution shapes the input current as a square wave, as in **Figure 2**.

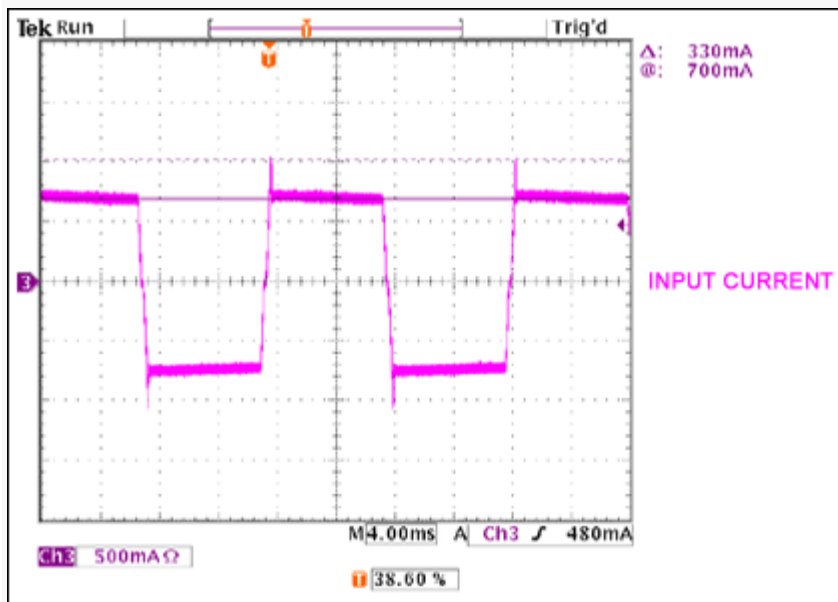


Figure 2. Input current for the LED driver.

Shaping the input current as a square is the best solution for control: it keeps its value (i.e., the transformer and dimmer load current) above the required minimum for the whole cycle of the line voltage.

This control is obtained using components R8 (sense resistor), R7, and C9. R7 and C9 provide the average MOSFET current, which is the same as the average input current; the MAX16834 maintains this value constant throughout each cycle of the input voltage.

Since this solution does not include electrolytic capacitors, the LED current is a rectified sinusoid (without dimmer) or a rectified sinusoid cut for a part of the angle (with dimmer), because energy is not stored between one cycle of the AC voltage and the

following (Figure 3).

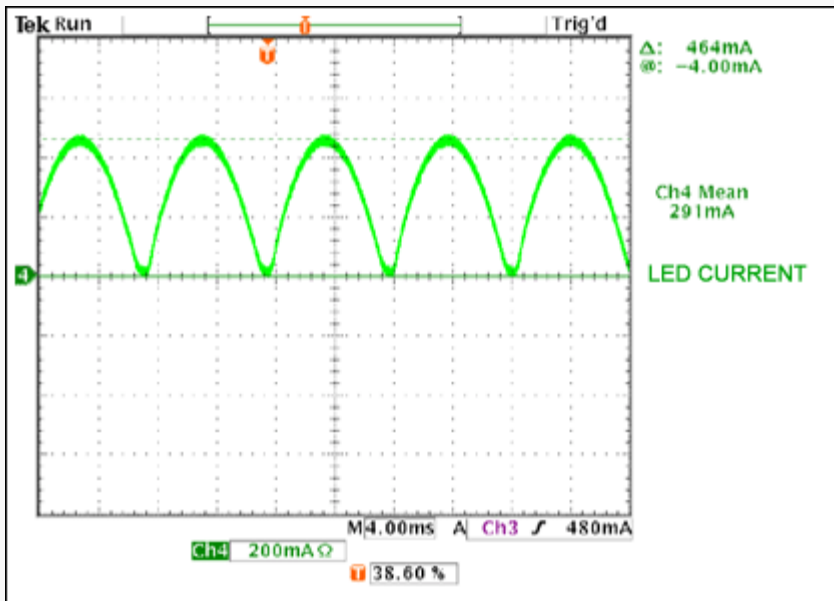


Figure 3. LED current is a rectified sinusoid, with frequency equal to twice the line voltage frequency.

The MAX16834 features output overvoltage protection (OVP). With OVP, if the LEDs are disconnected or open the driver turns off and the driver is not damaged.

Test results

This reference design board was tested under these conditions:

- Electronic transformer: Lightech LET-60
- Input voltage of the electronic transformer: 120VAC, 60Hz
- Input voltage of the driver circuit: 12VAC, 60Hz modulated at 40kHz
- Output: 4 series LEDs

We measured (without dimmer):

- LED power: 4.2W
- Efficiency: 77%
- Input power factor: 0.943

This design is compatible with these electronic transformers.

Input Voltage	Maker	Model
120VAC	B+L Technologies	FX95100
120VAC	Eaglerise Electric & Electronic (Foshan) Co Ltd.	B04558F1
120VAC	Q Tran®, Inc.	QT10-120/12-NTP-RC
120VAC	Hatch	RS1260M-LED
120VAC	Hatch	VS12-60WD
120VAC	Hatch	VS12-75WD
120VAC	Hatch	RS12-60PILB-LED
120VAC	Hatch	RS12-80m
120VAC	Hatch	RS12-15m
120VAC	Hatch	RS12-30m
120VAC	Lightech	LET-60
120VAC	Lightech	LVT-60
110VAC	Nobile	AFM-70KC
120VAC	Progress Lighting®	P8560-31
120VAC	Wang House Technology	WH-801E6A
120VAC	Wang House Technology	WH-601E2CA-2M
220VAC	Hatch	RS12-60-230m
220VAC	Leadman Electronics®	KY-05036S-12
220VAC	Ly SHLY	021-66770066
220VAC	Nobile	EN-35M
230VAC	Nobile	EN-35ST
230VAC	Nobile	EN-60D2
80-270VAC	NVC® Lighting Technology Corporation	NLD-15W/12V
220VAC	OSRAM®	ECO-ET 60/220

In addition, this solution has been tested to work with the following dimmer/electronic transformer combinations.

Input Voltage	Dimmer Maker	Dimmer Model	Electronic Transformer
120V	Lutron® Electronics	Nova NELV-450	Hatch R12-60M-LED
			B + L FX95100
120V	Lutron Electronics	Skylark SELV-300P	B + L FX95100
120V	Lutron Electronics	Diva DVELV-300P	Hatch R12-80M
			B + L FX95100

This solution has been tested to work correctly with the following dimmer/magnetic transformer combinations.

Input Voltage	Dimmer Maker	Dimmer Model	Magnetic Transformer
120V	Lutron Electronics	Nova NLV-600	Q Tran Qt10-120-12-NTP-PC10VA
			Eaglerise B04558F1 40VA
			Schneider Electric® 150VA150SV43A (Square D)
120V	Lutron Electronics	Diva DLV-600P	Q Tran Qt10-120-12-NTP-PC10VA
			Eaglerise B04558F1 40VA
120V	Lutron Electronics	Skylark SLV-600P	Q Tran Qt10-120-12-NTP-PC10VA
120V	Lutron Electronics	Maestro MALV-600	Q Tran Qt10-120-12-NTP-PC10VA
			Schneider Electric 150VA150SV43A (Square D)

Test procedure

- Turn off the 120VAC/230VAC power supply.
- Connect the input of the trailing-edge dimmer (if present) to the power supply.
- Connect the output of the dimmer to the input of the electronic transformer. Alternatively, connect the input of the transformer to the power supply if no dimmer is present.
- Connect the output of the dimmer to the V_{IN1} and V_{IN2} board inputs.
- Connect the LEDs between LED+ (anode) and LED- (cathode).
- Turn on the power supply.

Leadman Electronics is a registered trademark of Leadman Electronics International Inc.

Lutron is a registered trademark of Lutron Electronics Co., Inc.

NVC is a registered trademark of HUIZHOU NVC Industrial Development Co., Ltd. Corporation China.

OSRAM is a registered trademark of Osram Gesellschaft mit beschränkter Haftung GMBH Fed Rep Germany.

Progress Lighting is a registered trademark of Progress Lighting, Inc.

Q Tran is a registered trademark of Q Tran, Incorporated.

Schneider Electric is a registered trademark of Schneider SA Corporation France.

Related Parts

MAX16834 High-Power LED Driver with Integrated High-Side LED Current Sense and PWM Dimming MOSFET Driver -- [Free Samples](#)

Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest? [Sign up for EE-Mail™](#).

Application note 4708: www.maxim-ic.com/an4708

More information

For technical support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

AN4708, AN 4708, APP4708, Appnote4708, Appnote 4708

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal